
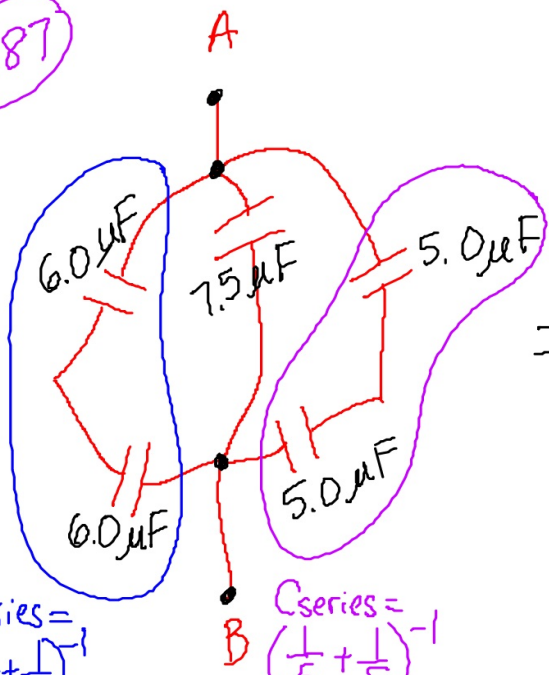


#87

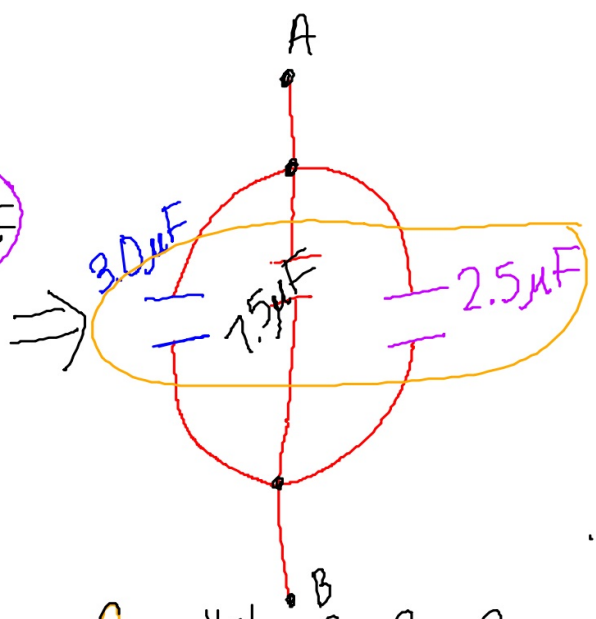

$$C_{\text{series}} = \left(\frac{1}{6} + \frac{1}{6}\right)^{-1} = 3.0 \mu\text{F}$$

$$C_{\text{series}} = \left(\frac{1}{5} + \frac{1}{5}\right)^{-1} = 2.5 \mu\text{F}$$



$$C_{\text{parallel}} = C_1 + C_2 + C_3 = 3.0 \mu\text{F} + 7.5 \mu\text{F} + 2.5 \mu\text{F} = 13 \mu\text{F}$$

### Energy in Capacitors

$$PE_E = \frac{1}{2} QV = \frac{1}{2} CVV = \frac{1}{2} CV^2 = \frac{1}{2} C \frac{Q^2}{C^2} = \frac{1}{2} \frac{Q^2}{C}$$

$$Q = CV \quad V = \frac{Q}{C}$$

#95

$$\frac{1}{2} CV^2 = \frac{1}{2} (20.0 \times 10^{-6} \text{F})(12.0 \text{V})^2 = 1.44 \times 10^{-3} \text{J} \text{ or } 1.44 \text{mJ}$$

#96

$$\frac{1}{2} QV = \frac{1}{2} (20.0 \times 10^{-6} \text{C})(9.0 \text{V}) = 9.0 \times 10^{-5} \text{J} \text{ or } 90 \mu\text{J}$$

#97

$$\frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(40.0 \mu\text{C})^2}{(80.0 \mu\text{F})} = 1.0 \times 10^{-5} \text{J} \text{ or } 10 \mu\text{J}$$

#98

$$PE_E = 2.00 \text{ J}$$

$$C = 10.0 \mu\text{F}$$

$$V = \text{---} \text{ V}$$

$$PE_E = \frac{1}{2} CV^2 \implies V = \sqrt{\frac{2PE_E}{C}}$$

$$2.00 \text{ J} = \frac{1}{2} (10.0 \mu\text{F}) V^2$$

$$V = 632 \text{ V}$$