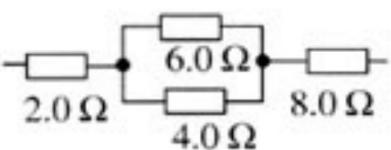


$$R_s = 4.0\Omega + 4.0\Omega \\ = 8.0\Omega$$

$$R_s = 2.0\Omega + 2.0\Omega \\ = 4.0\Omega$$

$$R_p = \left(\frac{1}{8.0\Omega} + \frac{1}{4.0\Omega} \right)^{-1}$$


$$= 2.7\Omega$$



$$R_s = 2 + 8 = 10\Omega$$

$$R_p = \left(\frac{1}{6} + \frac{1}{4} \right) = 2.4$$

$$R_t = R_s + R_p$$

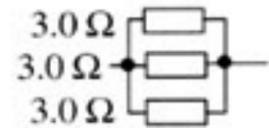

$$\left(\frac{1}{3} + \frac{1}{3} + \frac{1}{3} \right)^{-1} \\ = 1.5\Omega$$

$$R_t = 10 + 2.4 = 12.4\Omega$$

What is the resistance between A and B in Figure 5.26?

$$R_s = 10\Omega + 20\Omega + 20\Omega \\ = 50\Omega$$

$$(10\Omega + 10\Omega) + \left[\left(\frac{1}{20\Omega} + \frac{1}{30\Omega} \right) \right]^{-1}$$

$$20\Omega + 18.8\Omega = 38.8\Omega = 39\Omega$$

Each resistor in Figure 5.27 has a value of 6.0Ω . Calculate the resistance of the combination.

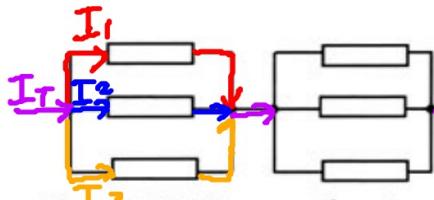


Figure 5.27 For question 3.

$$\left(\frac{1}{6} + \frac{1}{6} + \frac{1}{6} \right)^{-1} + \left(\frac{1}{6} + \frac{1}{6} + \frac{1}{6} \right)^{-1}$$

$$= 2\Omega + 2\Omega$$

$$= 4.0\Omega$$

You are given one hundred 1Ω resistors. What is the smallest and largest resistance you can make in a circuit using these?

100 1Ω resistors

Series circuit resistance = $(1+1+1+\dots)$

Parallel circuit

$$(1+1+1+\dots)^{-1} = (100)^{-1} \\ = (10 \cdot 10^2)^{-1} = 1.0 \cdot 10^{-2} \text{ parallel} \\ = 0.01$$

(100Ω)
for series
 $\leq 1.0 \cdot 10^2$


Q

A wire that has resistance R is cut into two equal pieces. The two parts are joined in parallel. What is the resistance of the combination?

$$\left(\frac{1}{\frac{R}{2}} + \frac{1}{\frac{R}{2}} \right)^{-1} = R_T$$

$$R = \frac{\rho L}{A}$$


$R \propto L$

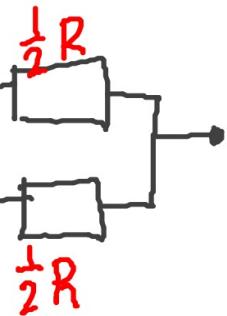

$$\left(\frac{2}{R} + \frac{2}{R} \right)^{-1} = \left(\frac{4}{R} \right)^{-1} = \frac{R}{4}$$

Bc it says the wire was split
in 2 equal parts

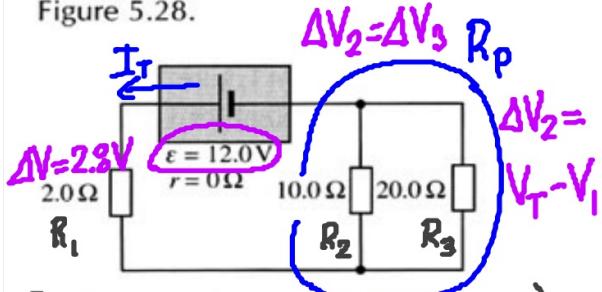Find the current in, and potential difference across, each resistor in the circuits shown in Figure 5.28.



	V	I	R
R_1	2.8V	1.4A	2.0Ω
R_2	9.2V	.92A	10.0Ω
R_3	9.2V	.46	20.0Ω
Total	12V	1.4A	8.7Ω

① Find R_T (equivalent resistance)

R_2 & R_3 are in parallel so

$$R_p = \left(\frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left(\frac{1}{10} + \frac{1}{20} \right)^{-1} = 6.7\Omega$$

R_p is in series with R_1 , so

$$R_T = R_1 + R_p = 2 + 6.7 = 8.7\Omega$$

$$I_T = I_1 \text{ b/c } R_1 \text{ is in series}$$

$$V_1 = I_1 R_1 = (1.4A)(2.0\Omega) \\ = 2.8V$$

$V_2 = V_3$ b/c R_2 & R_3 are ||


$$\text{so } V_2 = V_T - V_1 = 12 - 2.8$$

$$\textcircled{2} \text{ Find } I_T \rightarrow I_T = \frac{V_T}{R_T} = \frac{12V}{8.7\Omega} = 1.4A$$

$$I_2 = \frac{V_2}{R_2} = \frac{9.2V}{10.0\Omega} = .92A$$

$$I_3 = \frac{V_3}{R_3} = \frac{9.2V}{20.0\Omega} = .46A$$

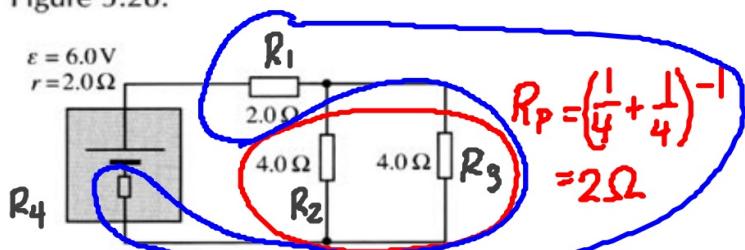Find the current in, and potential difference across, each resistor in the circuits shown in Figure 5.28.



$$R_T = ? \Omega$$

$$R_T = R_1 + R_4 + R_P$$

$$R_T = 6.0\Omega$$

$$I_T = ? A$$

$$I_T = \frac{V_T}{R_T} = \frac{6.0V}{6.0\Omega} = 1.0A$$

• B/c R_2 & R_3 are in parallel $V_2 = V_3$

$$\text{so } V_2 = V_T - V_1 - V_4$$

$$= 2.0V$$

$$\therefore I_2 = \frac{V_2}{R_2} = .5A$$

$$I_3 = \frac{V_3}{R_3} = .5A$$


	V	I	R
R_1	2.0V	1.0A	2.0Ω
R_2	2.0V	.5A	4.0Ω
R_3	2.0	.5A	4.0Ω
R_4	2.0V	1.0A	2.0Ω
Total	6.0V	1.0A	6.0Ω

• $I_T = I_1 = I_4$ b/c R_1 & R_4 are in series

$$\cdot V_1 = I_1 R_1 = 2.0V$$

$$\cdot V_4 = I_4 R_4 = 2.0V$$

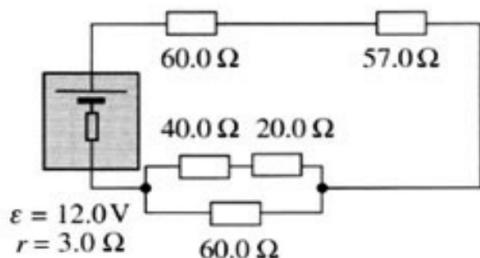Find the current in each of the resistors in the circuit shown in Figure 5.29. What is the total power dissipated in the circuit?



$$R_T = 60.0 + 57.0 + (1/60.0 + 1/(40.0 + 20.0))^{-1} + 3.0$$

$$R_T = 150 \text{ ohms}$$

$$P = (V^2)/R = (12.0 \text{ V})^2/(150 \text{ ohms}) = 0.96 \text{ W}$$