

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

AaBbCcI AaBbCcI AaBbCcI

Emphasis Heading 1 Normal

Clipboard

1 2 3 4 5 6

3. Rank the equivalent resistance of the five circuits below from greatest to least. Show each calculation clearly.

i. circuit 1

ii. circuit 2

iii. circuit 3

1. In which circuit above are meters properly connected to measure current through R1 and potential difference across R2? Explain.

Page: 1 of 3 Words: 442 90%

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

AaBbCcI AaBbCcI AaBbCcI

Emphasis Heading 1 Normal

Clipboard

1 2 3 4 5 6

2. Resistors R1 and R2 have an equivalent resistance of 6 ohms when connected in the circuit shown below. The resistance of R1 could be

(A) 1  $\Omega$   
 (B) 5  $\Omega$   
 (C) 8  $\Omega$   
 (D) 4  $\Omega$

Explain your answer choice.

$$6 = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$\frac{1}{6} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{6} - \frac{1}{8} > 0$$

v. circuit 5

Page: 1 of 3 Words: 442 100%

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

3. Rank the equivalent resistance of the five circuits below from greatest to least. Show each calculation clearly.

i. circuit 1

$R_T = 16\Omega$   
 $= 8 + 8$

ii. circuit 2

$R_T = 4\Omega$   
 $R_P = \left(\frac{1}{8} + \frac{1}{8}\right)^{-1}$

iii. circuit 3

4. In which circuit above are meters properly connected to measure current through R1 and potential difference across R2? Explain.

(1) (2) (3) (4)

Page: 1 of 3 Words: 442 100%

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

1. In which circuit above are meters properly connected to measure current through R1 and potential difference across R2? Explain.

2. Resistors R1 and R2 have an equivalent resistance of 6 ohms when connected in the circuit shown below. The resistance of R1 could be

(A) 1  $\Omega$   
(B) 5  $\Omega$   
(C) 8  $\Omega$   
(D) 4  $\Omega$   
Explain your answer choice.

iv. circuit 4

$\left(\frac{1}{2+4}\right) + \left(\frac{1}{3+3}\right)$   
 $\left(\frac{1}{4} + \frac{1}{4}\right)^{-1} = 6\Omega$

v. circuit 5

$\left(\frac{1}{1+3}\right) + \frac{1}{3}$   
 $1.7\Omega$

Page: 1 of 3 Words: 442 90%

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word


File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

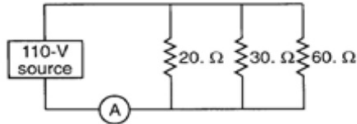
4. Three identical resistors have an equivalent resistance of 12 ohms when connected in series. What is the equivalent resistance if they are connected in parallel?

$12\Omega = R_T = R_1 + R_2 + R_3 = 3R$   
 $R = 4\Omega$   
 $R_p = \left(\frac{1}{4} + \frac{1}{4} + \frac{1}{4}\right)^{-1}$   
 $= 1.3\Omega$



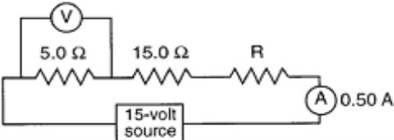5. The diagram above shows a parallel circuit.

- What is the equivalent resistance?
- What is the current measured by the ammeter?
- What is the voltage drop across each resistor?
- What is the current through each resistor?



Page: 2 of 3 Words: 442 90%

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

5. The diagram above shows a parallel circuit.



- What is the equivalent resistance? ✓
- What is the current measured by the ammeter? ✓
- What is the voltage drop across each resistor? ✓
- What is the current through each resistor?

(a)  $R_T = \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{60}\right)^{-1} = 10\Omega$

(b)  $I_T = \frac{V_T}{R_T} = \frac{110V}{10\Omega} = 11A$

(c) B/c the  $20\Omega$ ,  $30\Omega$ , and  $60\Omega$  resistor are in parallel they all have the same potential difference  $\Rightarrow 110V$

(d)  $I_{20\Omega} = \frac{110V}{20\Omega} = 5.5A$   $I_{30\Omega} = \frac{110V}{30\Omega} = 3.7A$   
 $I_{60\Omega} = \frac{110V}{60\Omega} = 1.8A$

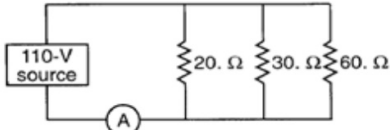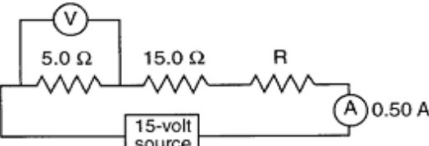6. Consider the series circuit shown above. A voltmeter and ammeter are connected as shown.

Page: 2 of 3 Words: 442 100% 3:38 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word


File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

Clipboard


1 2 3 4 5 6

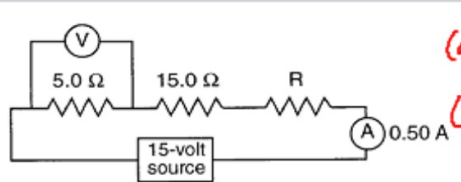

(a)  $V = IR = (0.50\text{A})(5.0\Omega) = 2.5\text{V}$   
 (b)  $V_T = I_T R_T$   $R = R_T - 5 - 15 \Rightarrow$   
 $15\text{V} = (0.50\text{A})R_T \Rightarrow R_T = 30\Omega$   $R = 10\Omega$

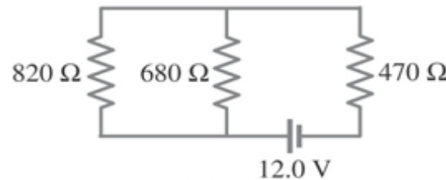6. Consider the series circuit shown above. A voltmeter and ammeter are connected as shown.

- What reading would the voltmeter show? ✓
- What is the value of the resistor R? ✓



7. Determine (a) the equivalent resistance of the circuit shown above, (b) the voltage across each resistor.

Page: 2 of 3 Words: 442 100% 3:41 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word


File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

Clipboard

1 2 3 4 5 6

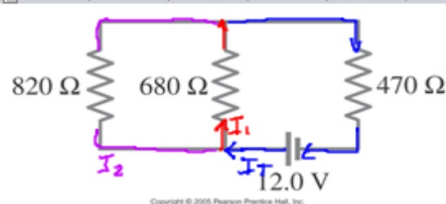

(a)  $R_T = 470\Omega + \left(\frac{1}{680} + \frac{1}{820}\right)^{-1} = 841.7\Omega$   
 (b)  $I_T = \frac{12.0\text{V}}{840\Omega} = 0.014\text{A}$   
 $V_{470\Omega} = (0.014\text{A})(470\Omega) = 6.58 = 6.6\text{V}$   
 $V_{680\Omega} = V_{820\Omega} = V_T - V_{470\Omega} = 12\text{V} - 6.6\text{V} = 5.4\text{V}$   
 (c)  $I_T = I_{470\Omega} = 0.014\text{A}$   
 $I_{680\Omega} = \frac{V_{680\Omega}}{R} = \frac{5.4\text{V}}{680\Omega} = 0.0079\text{A}$   $I_{820\Omega} = \frac{V_{820\Omega}}{R} = \frac{5.4\text{V}}{820\Omega} = 0.0066\text{A}$

7. Determine (a) the equivalent resistance of the circuit shown above, (b) the voltage across each resistor, and (c) the current through each resistor.

8. Calculate the terminal voltage for a battery with an internal resistance of  $0.90\Omega$  and an emf of  $8.50\text{V}$  when the battery is connected in series with (a) an  $81.0\text{-}\Omega$  resistor, and (b) a  $810.0\text{-}\Omega$  resistor.

9. What is the internal resistance of a  $12.0\text{-V}$  car battery whose terminal voltage drops to  $8.4\text{ V}$  when the starter draws  $75\text{ A}$ ? What is the resistance of the starter?

Page: 2 of 3 Words: 442 100% 3:56 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

8. Calculate the terminal voltage for a battery with an internal resistance of  $0.90\Omega$  and an emf of  $8.50\text{V}$  when the battery is connected in series with (a) an  $81.0\text{-}\Omega$  resistor, and (b) a  $810.0\text{-}\Omega$  resistor.

(a)  $V_T = \mathcal{E} - Ir$   $\mathcal{E} = I_T R_T \Rightarrow I_T = \frac{\mathcal{E}}{R_T} = \frac{\mathcal{E}}{R + r} = \frac{8.50\text{V}}{81 + .9} = .1038\text{A}$   $V_T = 8.4\text{V}$  (a)

$= 8.50 - (.1038\text{A})(.9\Omega)$

X What is the internal resistance of a  $12.0\text{-V}$  car battery whose terminal voltage drops to  $8.4\text{V}$  when the starter draws  $75\text{A}$ ? What is the resistance of the starter?

(b)  $V_T = \mathcal{E} - Ir$   $I_T = \frac{8.50}{810 + .9} = .01048\text{A}$

$= 8.50 - (.01048\text{A})(.9)$

$= 8.49\text{V} \Rightarrow V_T = 8.5\text{V}$  (b)

10. A  $5.0\text{-ohm}$  resistor, a  $20.0\text{-ohm}$  resistor, and a  $24\text{-volt}$  source of potential difference are connected in parallel. A single ammeter is placed in the circuit to read the total current.

Page: 2 of 3 Words: 442 100% 4:03 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

9. What is the internal resistance of a  $12.0\text{-V}$  car battery whose terminal voltage drops to  $8.4\text{V}$  when the starter draws  $75\text{A}$ ? What is the resistance of the starter?

$\mathcal{E} = 12.0\text{V}$   $\mathcal{E} = I_T R_T$   $V = \mathcal{E} - Ir$  (i)

$\Delta V_T = 8.4\text{V}$   $\mathcal{E} = I_T (R + r)$   $\therefore r = \frac{V - \mathcal{E}}{-I} = \frac{(8.4\text{V})(12.0\text{V})}{-(75\text{A})} = .048\Omega$

$I = 75\text{A}$   $\therefore R = \frac{\mathcal{E}}{I_T} - r$   $= \frac{(12.0\text{V})}{75\text{A}} - .048\Omega = .112\Omega = .11\Omega$  (ii)

10. A  $5.0\text{-ohm}$  resistor, a  $20.0\text{-ohm}$  resistor, and a  $24\text{-volt}$  source of potential difference are connected in parallel. A single ammeter is placed in the circuit to read the total current.

- On the diagram below, draw in wires connecting the components shown to make a complete circuit that will function as described above.

$5.0\Omega$

Page: 2 of 3 Words: 442 100% 4:08 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word


File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

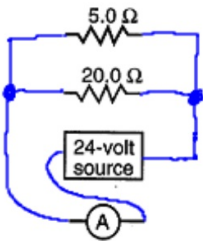10. A 5.0-ohm resistor, a 20.0-ohm resistor, and a 24-volt source of potential difference are connected in parallel. A single ammeter is placed in the circuit to read the total current.

- On the diagram below, draw in wires connecting the components shown to make a complete circuit that will function as described above.



(a)  $R_T = \left(\frac{1}{5} + \frac{1}{20}\right)^{-1} = 4.0\Omega$





(b)  $I_T = \frac{V_T}{R_T} = \frac{24V}{4.0\Omega} = 6.0A$

- Determine the total resistance. (a)
- Determine the total current measured by the ammeter. (b)

11. Three 240-Ω resistors can be connected together in four different ways, making combinations of series and/or parallel circuits. What are these four ways, and what is the net resistance in each case?

Page: 3 of 3 Words: 442 100% 4:12 PM

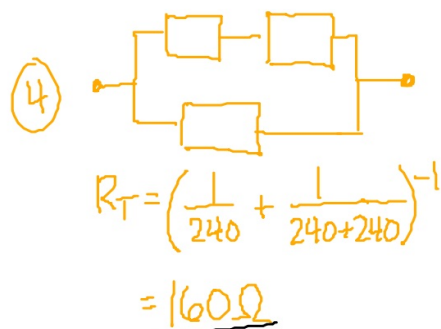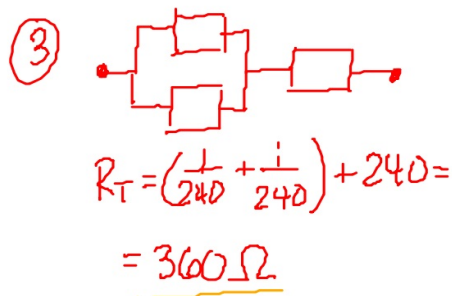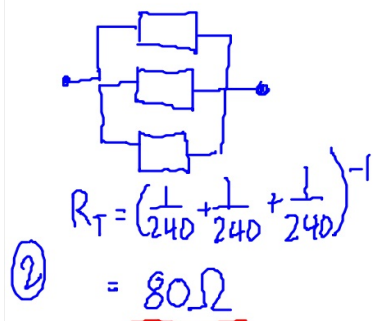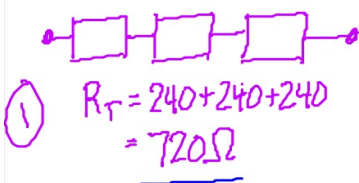8. Three 240-Ω resistors can be connected together in four different ways, making combinations of series and/or parallel circuits. What are these four ways, and what is the net resistance in each case?



IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

11. Three 240-Ω resistors can be connected together in four different ways, making combinations of series and/or parallel circuits. What are these four ways, and what is the net resistance in each case?

12. Complete a V-I-R chart for the circuit shown below.

$$R_T = \left( \frac{1}{10} + \frac{1}{2 + \left( \frac{1}{6} + \frac{1}{9} \right)^{-1}} \right)^{-1}$$

$$R_T = 3.6 \Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{9V}{3.6 \Omega} = 2.5 A$$

$$V_T = V_{10\Omega} = 9V \Rightarrow I_{10\Omega} = \frac{V_T}{R} = \frac{9.0V}{10\Omega} = 0.9 A$$

$$I_1 = I_T - I_2 = 2.5 - 0.9 = 1.6 A$$

$$I_3 = \frac{V}{R} = \frac{5.8V}{6\Omega} = 0.97 A$$

$$I_4 = \frac{5.8V}{9.0\Omega} = 0.64 A$$

$$V_{2\Omega} = I_1 R = (1.6 A)(2\Omega) = 3.2 V$$

Page: 3 of 3 Words: 33/442 100% 4:26 PM

IB Physics SL Y2 – Electric Circuits Homework Problems.doc [Compatibility Mode] - Microsoft Word

File Home Insert Page Layout References Mailings Review View

Calibri 11

Font Paragraph Styles

13. Three resistors are connected in parallel as shown above. What is the total power dissipated?

$$V_T = 110V$$

$$R_T = 10\Omega$$

$$P = \frac{V^2}{R} = \frac{(110V)^2}{(10\Omega)} = 1210W$$

14. Three resistors are connected in series as shown above. What is the total power dissipated?

$$V_T = 9.0V$$

$$R_T = 8.0\Omega + 2.0\Omega + 12.0\Omega = 22\Omega$$

$$P = \frac{V^2}{R} = \frac{(9.0V)^2}{22\Omega} = 3.7W$$

Page: 3 of 3 Words: 33/442 100% 4:28 PM