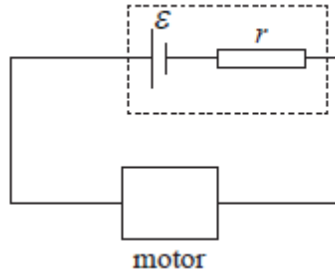


Name: _____ Date: _____ Period: _____

Objectives:

- 5.1 Electric potential difference, current, and resistance
- 5.2 Electric circuits

1. A cell of emf ϵ and internal resistance r delivers current to a small electric motor.




450 C of charge flows through the motor and 9000 J of energy are converted in the motor. 1800 J are dissipated in the cell. The emf of the cell is

- A. 4.0 V.
 - B. 16 V.
 - C. 20 V.
 - D. 24 V.
2. A cylindrical conductor of length l , diameter D and resistivity ρ has resistance R . A different cylindrical conductor of resistivity 2ρ , length $2l$ and diameter $2D$ has a resistance

- A. $2R$
- B. R
- C. $\frac{R}{2}$
- D. $\frac{R}{4}$

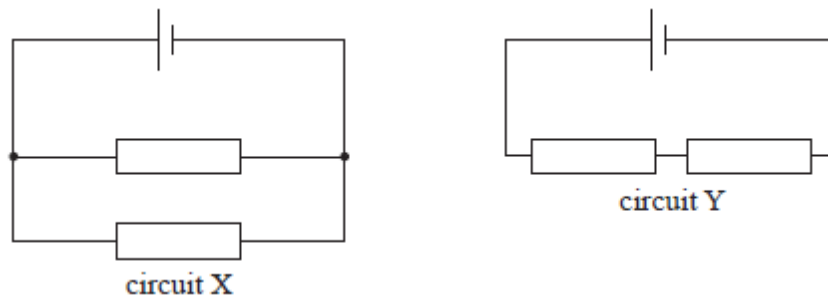3. In the circuits below the cells have the same emf and zero internal resistance. The resistors all have the same resistance.




Which of the following gives the ratio $\frac{\text{power dissipated in X}}{\text{power dissipated in Y}}$?

- A. $\frac{1}{4}$
- B. $\frac{1}{2}$
- C. 1
- D. 4

4. Two rectangular blocks, X and Y, of the same material have different dimensions but the same overall resistance. Which of the following equations is correct?

- A. $\text{resistivity of X} \times \text{length of X} = \text{resistivity of Y} \times \text{length of Y}$
- B. $\frac{\text{length of X}}{\text{cross sectional area of X}} = \frac{\text{length of Y}}{\text{cross sectional area of Y}}$
- C. $\text{resistivity of X} \times \text{cross sectional area of X} = \text{resistivity of Y} \times \text{cross sectional area of Y}$
- D. $\frac{\text{length of X}}{\text{cross sectional area of Y}} = \frac{\text{length of Y}}{\text{cross sectional area of X}}$

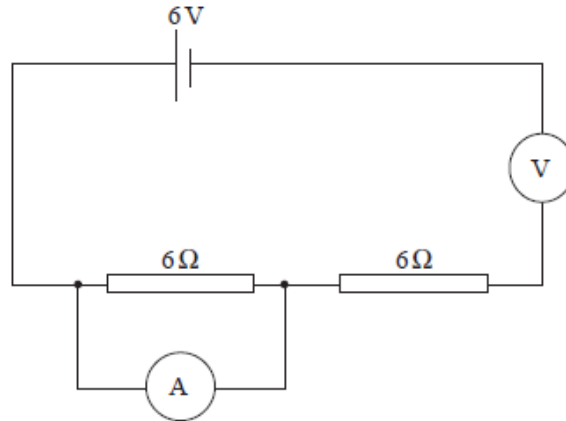
5. Two $6\ \Omega$ resistors are connected in series with a $6\ \text{V}$ cell. A student incorrectly connects an ammeter and a voltmeter as shown below.



The readings on the ammeter and on the voltmeter are

	Ammeter reading / A	Voltmeter reading / V
A.	0.0	0.0
B.	0.0	6.0
C.	1.0	0.0
D.	1.0	6.0

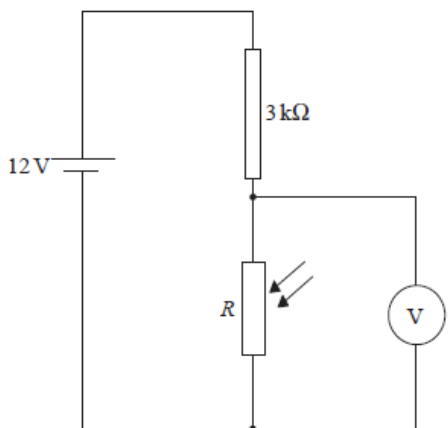6. The diagram shows a potential divider circuit.



In order to increase the reading on the voltmeter the

- A. temperature of R should be increased.
- B. temperature of R should be decreased.
- C. light intensity on R should be increased.
- D. light intensity on R should be decreased.

Part 2 Electrical resistance and electric circuits

- (a) Define *resistance* and state Ohm's law. [2]

Resistance:

.....

Ohm's law:

.....

- (b) A resistor made from a metal oxide has a resistance of $1.5\ \Omega$. The resistor is in the form of a cylinder of length $2.2 \times 10^{-2}\text{ m}$ and radius $1.2 \times 10^{-3}\text{ m}$. Calculate the resistivity of the metal oxide. [2]

.....

.....

.....

.....


- (c) The manufacturer of the resistor in (b) guarantees its resistance to be within $\pm 10\%$ of $1.5\ \Omega$ provided the power dissipation in the resistor does not exceed 1.0 W . Calculate the maximum current in the resistor for the power dissipation to be equal to 1.0 W . [2]

.....

.....

(This question continues on the following page)

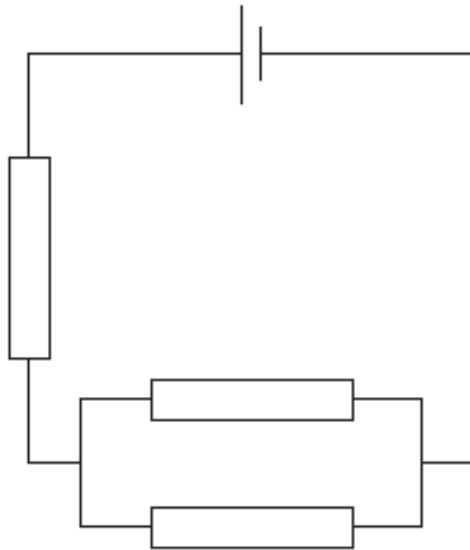- (d) The resistance of each of the resistors in the circuit below is measured to be $1.5\ \Omega$ with an accuracy of $\pm 10\%$.



The cell has an emf of 2.0 V and negligible internal resistance.

- (i) Define *emf*. [1]

.....
.....

- (ii) Determine the minimum and the maximum power that could be dissipated in this circuit. [3]

.....
.....
.....
.....
.....